



Chettinad College of Engineering and Technology

Karur-639114

FLIPFLOPS


J.JENISHA

ASSISTANT PROFESSOR

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Overview

- Latches respond to trigger levels on control inputs
 - **Example:** If $G = 1$, input reflected at output
- Difficult to precisely time when to store data with latches
- Flip flops store data on a rising or falling trigger edge.
 - **Example:** control input transitions from 0 -> 1, data input appears at output
 - Data remains stable in the flip flop until next rising edge.
- Different types of flip flops serve different functions
- Flip flops can be defined with characteristic functions

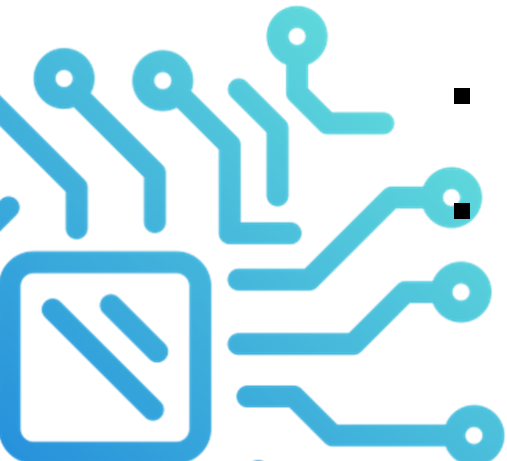

D Flip-Flop

- Stores a value on the positive edge of C
- Input changes at other times have no effect on output

Positive edge triggered





D gets latched to Q on the rising edge of the clock.



Clocked D Flip-Flop

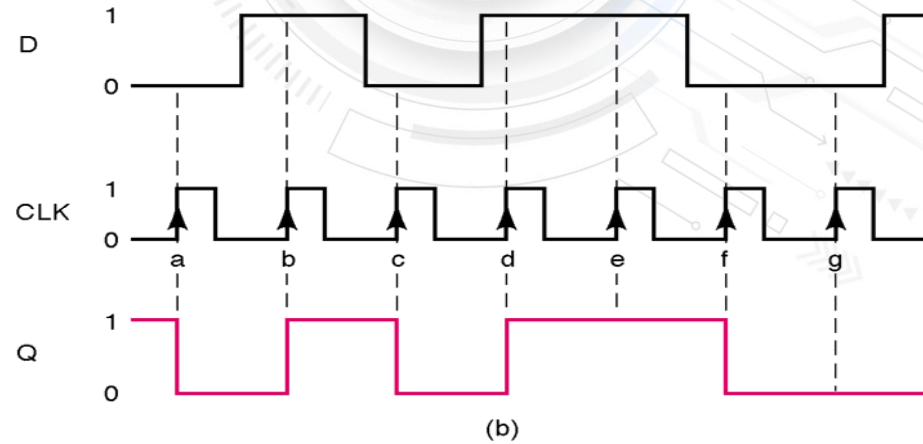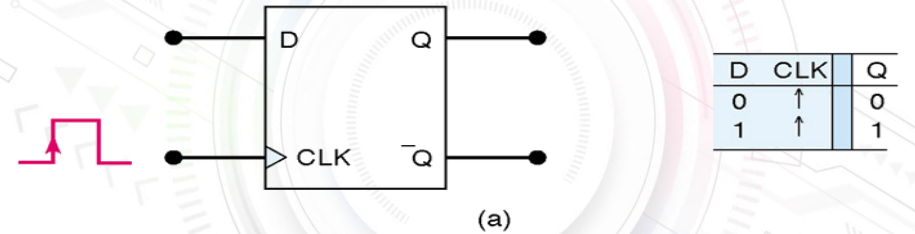- Stores a value on the positive edge of C
- Input changes at other times have no effect on output



Positive and Negative Edge D Flip-Flop

- D flops can be triggered on positive or negative edge
- Bubble before *Clock (C)* input indicates negative edge trigger


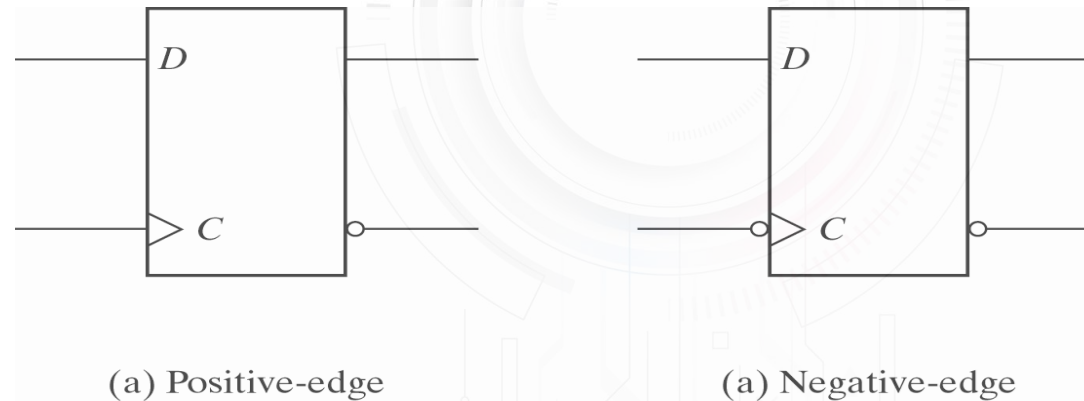


Fig. 5-11 Graphic Symbol for Edge-Triggered *D* Flip-Flop

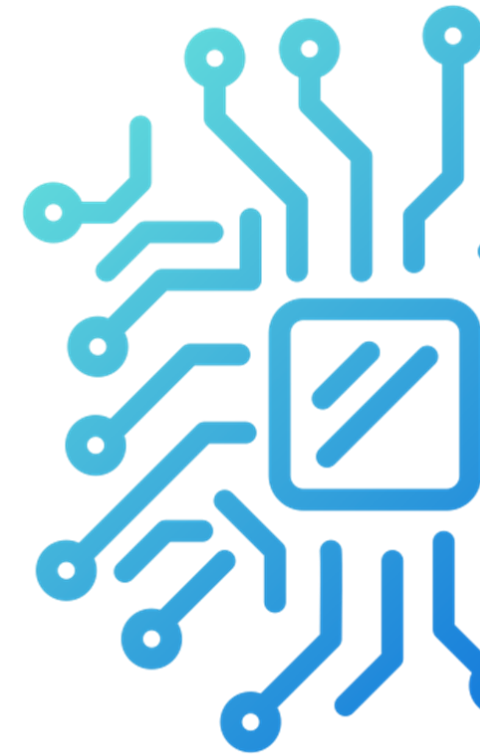

Positive Edge-Triggered J-K Flip-Flop

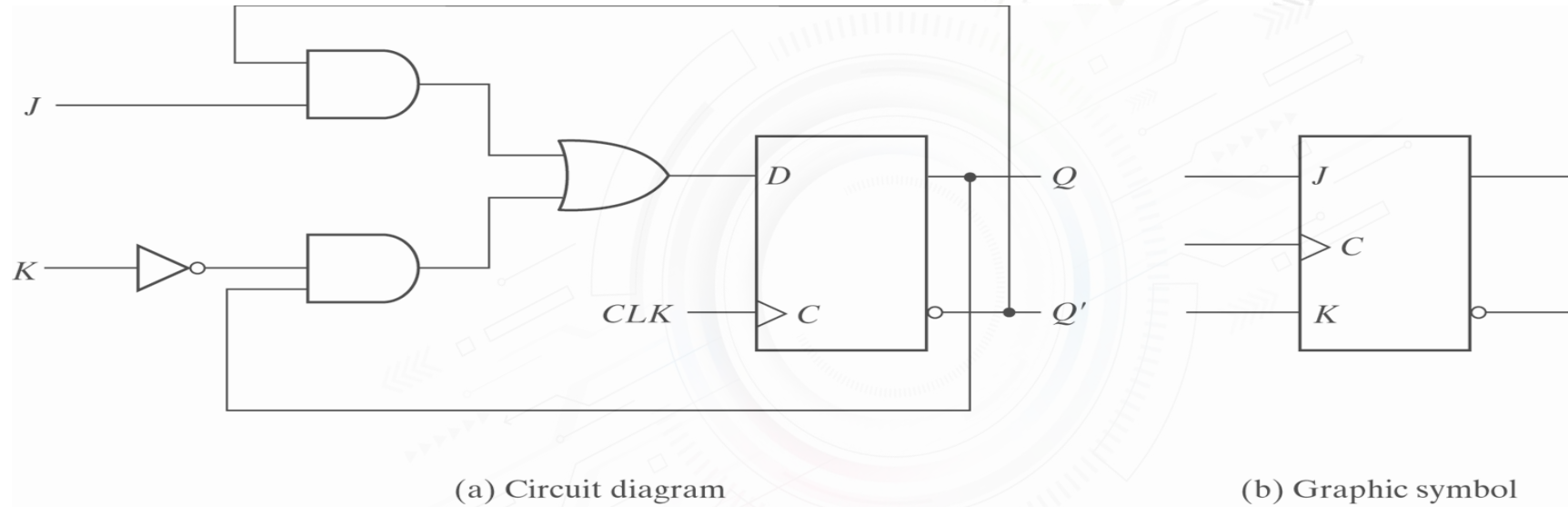



Fig. 5-12 JK Flip-Flop

Created from D flop
J sets
K resets
J=K=1 -> invert output



Clocked J-K Flip Flop

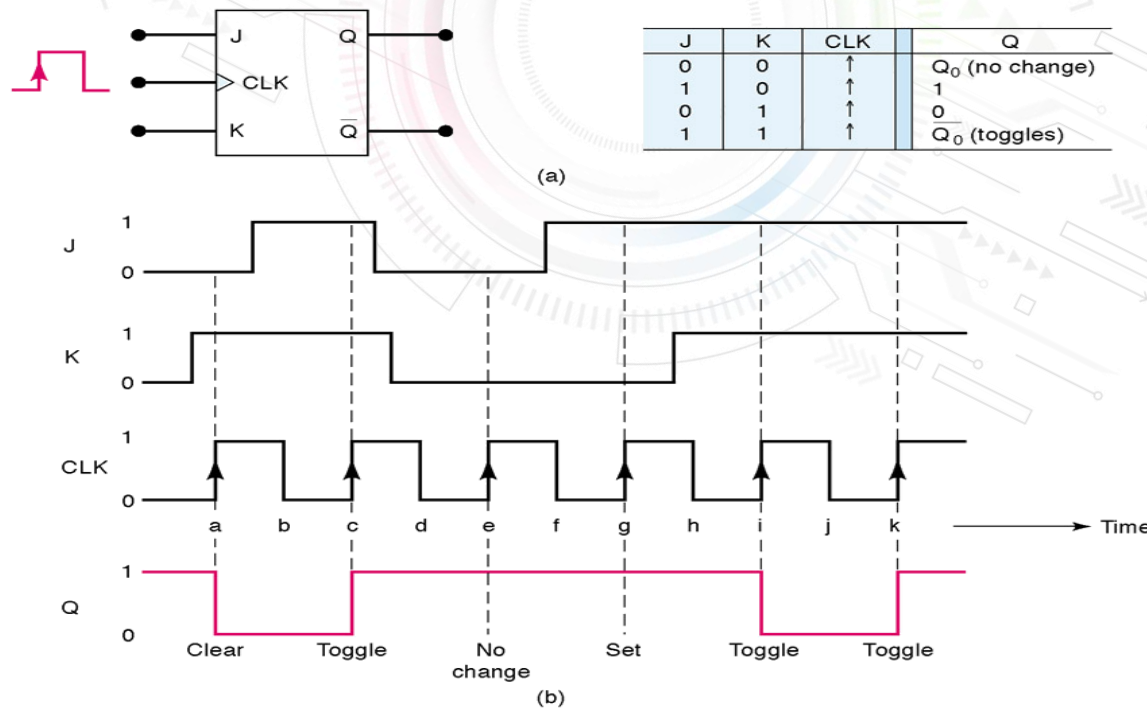- Two data inputs, J and K
- J -> set, K -> reset, if J=K=1 then toggle output



JK FLIPFLOP OUTPUT



| CLK | J | K | Q_n | Q_{n+1} | Q_{n+1} |
|-----|--------|--------|--------|-----------|-----------|
| 0 | X | X | 0/1 | 0/1 | Q_n |
| ↑ | 0 0 | 0 0 | 0 1 | 0 1 | Q_n |
| ↑ | 0 0 | 1 1 | 0 1 | 0 0 | 0 |
| ↑ | 1 1 | 0 0 | 0 1 | 1 1 | 1 |
| ↑ | 1 1 | 1 1 | 0 1 | 1 0 | Q_n' |

Positive Edge-Triggered T Flip-Flop

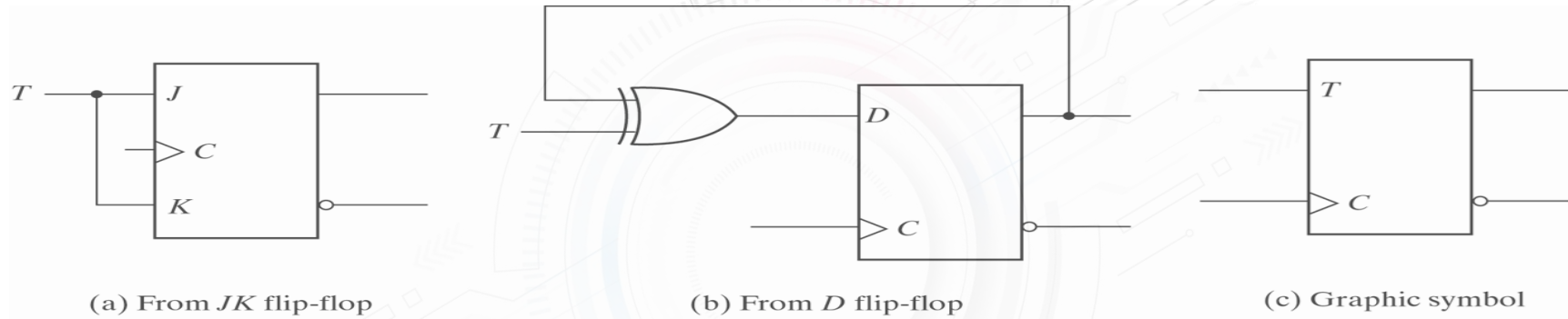


Fig. 5-13 T Flip-Flop

Created from D flop
T=0 -> keep current
K resets
T=1 -> invert current

| Q_t | $Q(t+1)$ | T |
|-------|----------|---|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

Summary

- Flip flops are powerful storage elements
 - They can be constructed from gates and latches!
- D flip flop is simplest and most widely used
- Asynchronous inputs allow for clearing and presetting the flip flop output
- Multiple flops allow for data storage
 - The basis of computer memory!
- Combine storage and logic to make a computation circuit.