

# **Department of Electrical and Electronics Engineering EE8017- High Voltage Direct Current Transmission Unit II - MCQ Bank**

- 1. A 12-pulse bridge is preferred in HVDC because
- a) It eliminates certain harmonics
- b) It results in better power factor
- c) Series connection of converters on D.C. side is better Answer. a)
- 2. Fault on a two terminal DC link is removed by
- a) Breakers on DC side
- b) Breakers on AC side
- c) Current control of converters

Answer. C)

- 3. In HVDC converters, the thyristor are connected in series
- a) To provide the required current rating, and they are turned on at the same instant.
- b) To provide the required current rating, and they are turned on at different instants.
- c) To provide the required voltage rating, and they are turned on at the same instant.
- d) To provide the required voltage rating, and they are turned on at different instants.

- 4. The minimum possible value of transformer utilization factor is
- a) 1.571
- b) 1.481
- c) 1.391

d) 1.690

Answer: b)

- 5. Which of the following sentences is/are correct?
- 1. High speed power reversal without the requirement of mechanical switching is possible in series MTDC system by reversal of the DC voltage polarity.
- 2. High speed power reversal without the requirement of mechanical switching is possible in parallel MTDC system by reversal of the DC voltage polarity.
- 3. Series MTDC system has the advantage of possibility of staged development.
- 4. Parallel MTDC system has the advantage of possibility of staged development.
- 5. Insulation coordination is a problem in series MTDC system.
- 6. Insulation coordination is a problem in parallel MTDC system.
- 7. Permanent fault in a line would lead to complete shutdown in a series MTDC system.
- 8. Permanent fault in a line would lead to complete shutdown in a parallel MTDC system.

In Options

- a) 1,4,5 and 7
- b) 2,4,3 and 6
- c) 2.4,3 and 8
- d) 1,2,3 and 6

Answer: a)

- 3. The three phase voltage at the AC side terminals of the 6 pulse LCC is sinusoidal and balanced, and there is a constant current source on the DC side. Which of the following sentences is/are correct about following?
- 1) In a 6 pulse LCC, the 11th order harmonic component in the AC side currents is a characteristic harmonic.
- 2) In a 6 pulse LCC, the 25th order harmonic component in the AC side currents is a noncharacteristic harmonic.
- 3) In a 6 pulse LCC, the 2nd order harmonic component in the AC side currents is a characteristic harmonic.
- 4) In a 6 pulse LCC, the 4th order harmonic component in the AC side currents is a non-

characteristic harmonic.

Options

- a) 1 and 2
- b)1 and 4
- c) 2 and 3
- d) 2 and 4

Answer: b)

- 4. The three phase voltage at the AC side terminals of the 12 pulse LCC is sinusoidal and balanced, the transformers are ideal, and there is a constant current source on the DC side. Which of the following sentences is/are correct about following?
- 1. In a 12 pulse LCC, the 17th order harmonic component in the AC side currents is a characteristic harmonic.
- 2. In a 12 pulse LCC, the 19th order harmonic component in the AC side currents is a noncharacteristic harmonic.
- 3. In a 12 pulse LCC, the 35th order harmonic component in the AC side currents is a characteristic harmonic.
- 4. In a 12 pulse LCC, the 47th order harmonic component in the AC side currents is a noncharacteristic harmonic.

**Options** 

- a) 1 and 2
- b) 1 and 4
- c) 2 and 3
- d) 2 and 4

- 8) In HVDC converter station equipment using thyristor it is necessary to use a large number of thyristor in series because.
- a) Current ratings of thyristor are low.
- b) Voltage ratings of thyristor are low.
- c) Thyristor always fail to an internal open circuit.

d) None of the above.

Answer: b)

- 9) In the HVDC system, the ac harmonics which get effectively eliminated with 12 pulse bridge converters are..
- a) Triplen harmonics
- b) Triplen and 5th harmonics
- c) Triplen, 5th and 7th harmonics
- d)5th and 7th harmonics

Answer: d)

- 10) By which of the following method string efficiency can be improved?
- a) Using a guard ring
- b) Grading the insulator
- c) Using long cross arm
- d)All of the above

Answer: d) All of the above

- 11) The voltage drop, for constant voltage transmission is compensated by installing.
- a) Inductors
- b) Capacitors
- c) Synchronous motors
- d) All of above

Answer: c)

- 12) Asynchronous tie line is a
- a) AC transmission line

#### b)DC transmission line

- c) either 1 or 2
- d) none of the above

Answer: b)

- 13) Modern HVDC systems are all
- (a) 3-pulse converters
- (b) 6-pulse converters
- (c) 24-pulse converters
- (d) 12-pulse converters

Answer: d)

- 14) The HVDC protections are grouped to:
- a) DC protections
- b) AC protections ·
- c) Apparatus Protective Relays
- d)All of these

Answer: d)

- 15)12 Pulse converter is which type of converter
- a) Line Commutated Converter
- b) Voltage Source Converter
- c) Both a) and b)
- d) None

Answer: a)

- 16) Which type of connection on the secondary side of transformer-1 and transformer-II is used to obtain phase shift of 30 degrees in 12 pulses Converter?
- a) Star-Star
- b) Delta-Delta
- c) Delta-Star
- d)Star-Delta

Answer: d)

- 17) Which Multi Terminal DC link (MTDC) system is more reliable?
- a) Series MTDC

### b)Parallel MTDC

c) Both a) and b)

Answer: b)

- 18) Which statement are true about series MTDC system
- 1) High speed of reversal of power is possible without mechanical switching
- 2) More losses in line and in valves
- 3) The permanent fault in a line section would lead to complete shutdown
- 4) High speed of reversal of power is possible with mechanical switching Option:
- a) All of these
- b) Only 1
- c) Only1, 2 and 3
- d) Only 2,3 and 4

Answer: c)

- 19) Which statement are true about Parallel MTDC system
- 1) High speed of reversal of power is possible without mechanical switching
- 2) More losses in line and in valves
- 3) The permanent fault in a line section would lead to complete shutdown
- 4) High speed of reversal of power is possible with mechanical switching Option:
- a) All of these

#### b)Only 4

- c) Only1, 2 and 3
- d) Only 2,3 and 4

Answer: b)

- 20) The output voltage equation of 12 pulse converter is
- a)  $V_d = 2V_{d0} \cos \alpha$
- b)  $V_d = Vd_0 Cos\alpha$

- c)  $V_d = 0.5V_{d0} \cos \alpha$
- d)  $V_d = 3V_{d0} \cos \alpha$

Answer: a)

- 21) In HVDC transmission there are predominant
- a) Voltage harmonics on DC side and current harmonics on AC side of converters
- b) Current harmonics on DC side and voltage harmonics on AC side of converters
- c) Current harmonics only on the DC side of Converters
- d) Voltage harmonics only on the AC side of converters

Answer: a)

- 22) What are the sources of Harmonics?
- a) Power Electronic Application
- b) Non Linear Load
- c) Both a) and b)

Answer: c)

- 23) If the firing angle becomes negative, then the rectifier begins to work as
- a. A rectifier
- b. An inverter
- c. A chopper
- d. A regulator

Answer: b)

- 24) Transformer utilization factor is a measure of the merit of a rectifier circuit. It is the ratio of
- a. AC input power to the transformer volt amp rating required by secondary
- b. AC input power to the transformer volt amp rating required by primary
- c. DC output power to the transformer volt amp rating required by secondary
- d. DC output power to the transformer volt amp rating required by primary

- 25) Ripple factor is the ratio of
- a. Rms value of the ac component of load voltage to the dc voltage
- b. Average value of the ac component of load voltage to the peak value of voltage
- c. Average value of the dc component of load voltage to the ac voltage
- d. Peak value of the dc component of load voltage to the ac voltage

Answer: a)

- 26) Form factor of a rectifier is the ratio of
- a. Root mean square value of voltage and current to its peak value
- b. Root mean square value of voltage and current to its average value
- c. Average value of current and voltage to its root mean square value
- d. Peak value of current and voltage to its root mean square value Answer: b)
- 27.To detect an over current fault condition, the most reliable method is to connect a
- a. Current sensor across IGBT
- b. Voltage sensor across IGBT
- c. Current sensor in series with IGBT
- d. Voltage sensor in series with IGBT

Answer: c)

- 28) The on state voltage drop of IGBT consists of
- a. Drop across the collector junction
- b. Drop across the drift region
- c. Drop across MOSFET portion
- d. All of these

Answer: d.

- 29) Advantages of HVDC transmission over AC system is / are
- a. Reversal of power can be controlled by firing angle
- b. Very good dynamic behavior

- c. They can link two AC system operating un synchronized
- d. All of these

Answer: d)

- 30) Double edge modulation eliminates certain harmonics when the reference is a
- a. Sine wave
- b. Square wave
- c. Triangular wave
- d. Trapezoidal wave

Answer: a)

- 31) A 12-pulse converter consists of
- (a) two 6-pulse converters in series
- (b) two 6-pulse converters in parallel
- (c) (a) or (b)
- (d) (a) and (b)

Answer: a)

- 32) A pack in an IGBT valve comprises
- (a) triggering gate pulse circuit
- (b) parallel connect IGBTs
- (c) series and parallel connected IGBTs with projection
- (d) none of the above

Answer: c)

- 33)12-pulse converters are used in modern converters because of
- (a) reduced current
- (b) reduced ripple
- (c) increased voltage and reduced harmonics
- (d) both (b) and (c)

Answer: d)

lln 12-pulse connections, transformers are connected	
) Delta/Delta (both)	
) Star/Star (both)	
) Star/Delta (both)	
) One Star/Star and other Star/Delta	
nswer: d)	
(s) If pulse number = p, and k is an integer, voltage harmonic generated on the DC side is	
) pk + 1	
) pk – 1	
) 2pk	
)pk	
nswer: d)	
$\mathbf{S}$ ) If pulse number is = $\mathbf{p}$ and $\mathbf{k}$ is an integer, the voltage harmonic generated on the AC signals.	ide is
) pk	
) 2pk	
) pk ± 1	
) 2pk ± 1	
nswer: a)	
In a 12-pulse converter, the phase difference between the two 6-pulse bridges is	
) 0°	
) 60°	
) 30°	
) 15°	
nswer: c)	
The lowest current harmonic produced in 12-pulse converters is	
)11	
) 13	

- (c) 23
- (d) 25

Answer: a)

- 39)Increase in pulse number has the effect of
- (a) increasing harmonics
- (b) decreasing the harmonic number
- (c) increasing the lowest harmonic number
- (d) no effect

Answer: c)

- 40)In a 12-pulse bridge, if one transfers Y-Y has turns ratio 1:1, the other transformer Y-D will have turns ratio
- (a) 1:1
- (b) 1:3
- (c) 3:1
- (d) 1: 2

Answer: b)

- 41) Converter transformer act as a source of generation of harmonics because of
- (a) Magnetostiction
- (b) nonlinear nature of B-H curve of iron core
- (c) magnetising current
- (d) none of the above

- 42) Filters used in 12-pulse converters usually on the AC side are
- (a) 5th, 7th and high-pass
- (b) 11th, 13th and high-pass
- (c) 6th, 12th and high-pass
- (d) Only high-pass filter

## Answer: b)

- 43) For power frequency, the harmonic filter acts as a
- (a) leading p.f. load supplying leading kVA
- (b) lagging p.f. load supplying lagging kVA
- (c) (a) or (b) depending on the p.f. of the system
- (d) leading p.f. at rectifier end and lagging p.f. at inverter end

Answer: a)

- 44) The maximum value of the harmonic current depends on
- (a) fi ring angle
- (b) overlap angle
- (c) DC current
- (d) both firing angle and overlap angle

Answer: d)

- 45) Harmonic filters are protected by
- (a) overcurrent relays
- (b) lightning arresters
- (c) spark gaps
- (d) none of the above

Answer: b)

- 46)TIF factor usually lies between
- (a) 10 to 25
- (b) 20 to 30
- (c) 25 to 50
- (d) 50 to 100

- 47) Advantage of ground return in HV-bipolar DC system is
- (a) less power loss
- (b) can be built in stages
- (c) in the event of fault, 50% power is available
- (d) all of the above
- (e) none of the above

Answer: d)

- 48) The ground currents in HVDC system flow through
- (a) small area
- (b) small area along the line
- (c) very large area and does not confine to route of the line
- (d) very large area along the route of the line

Answer: c)

- 49) The earth electrode in the ground return DC line is located from the converter station at a distance of
- (a) 1 km
- (b) 3 to 5 km
- (c) 10 km
- (d)8 to 20 km

Answer: d)

- 50) The design of land electrode connected to the earth electrode depends on
- (a) current and operating time
- (b) heat dissipation and safety
- (c) current, operating time, life time, polarity, and safety
- (d) soil resistivity, thermal conductivity, safety, reliability, and electrode current