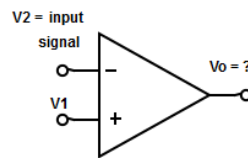


Department of Electrical and Electronics Engineering**EE8451-Linear Integrated Circuits & Applications****Unit II - MCQ Bank**

1. Determine the output from the following circuit



- A) 180° In Phase With Input Signal
- B) 180° Out Of Phase With Input Signal**
- C) Same As That Of Input Signal
- D) Output signal cannot be determined

Answer: (B)

2. Which of the following electrical characteristics is not exhibited by an ideal op-amp?

- A) Infinite Voltage Gain
- B) Infinite Bandwidth
- C) Infinite Output Resistance**
- D) Infinite Slew Rate

Answer: (C)

3. Ideal op-amp has infinite voltage gain because

- A) To Control The Output Voltage
- B) To Obtain Finite Output Voltage**
- C) To Receive Zero Noise Output Voltage
- D) None Of The Mentioned

Answer: (B)

4. Find the output voltage of an ideal op-amp. If V_1 and V_2 are the two input voltages

- A) $V_O = V_1 - V_2$
- B) $V_O = A \times (V_1 - V_2)$**
- C) $V_O = A \times (V_1 + V_2)$
- D) $V_O = V_1 \times V_2$

Answer: (B)

5. How will be the output voltage obtained for an ideal op-amp?

- A) Amplifies The Difference Between The Two Input Voltages**
- B) Amplifies Individual Voltages Input Voltages
- C) Amplifies Products Of Two Input Voltage
- D) None of the mentioned


Answer: (A)

6. Which is not the ideal characteristic of an op-amp?

- A) Input Resistance $\rightarrow 0$**
- B) Output Impedance $\rightarrow 0$
- C) Bandwidth $\rightarrow \infty$
- D) Open Loop Voltage Gain $\rightarrow \infty$

Answer: (A)

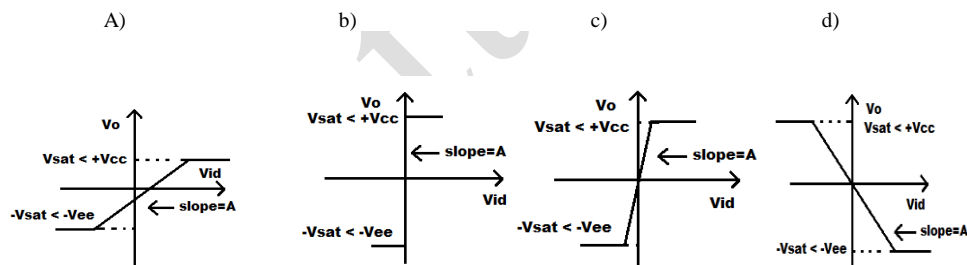7. Find the ideal voltage transfer curve of a normal op-amp.



Answer: (C)

8. Which factor determine the output voltage of an op-amp?

- A) Positive Saturation
- B) Negative Saturation

C) Both Positive And Negative Saturation Voltage

D) Supply Voltage

Answer: (C)

9. In which configuration does the op-amp function as a high gain amplifier?

A) Differential Amplifier

B) Inverting Amplifier

C) Non-Inverting Amplifier

D) All Of The Mentioned

Answer: (D)

10. How does the open loop op-amp configuration classified?

A) Based On The Output Obtained

B) Based On The Input Applied

C) Based On The Amplification

D) Based on the feedback network

Answer: (B)

11. What will be the voltage drop across the source resistance of differential amplifier when connected in open loop configuration?

A) Zero


B) Infinity

C) One

D) Greater Than One

Answer: a

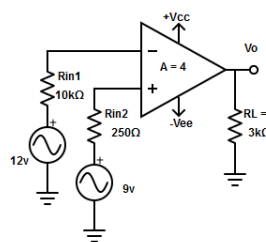12. Calculate the output voltage for the given circuit.



- A) $V_O = 7V$
- B) $V_O = 5.9V$
- C) $V_O = 12V$**
- D) $V_O = 11.4V$

Answer: (C)

13. What happen if any positive input signal is applied to open-loop configuration?

- A) Output Reaches Saturation Level**
- B) Output Voltage Swing's Peak To Peak
- C) Output Will Be A Sine Waveform
- D) Output Will Be A Non-Sinusoidal Waveform

Answer: a

14. Which of the following is not a feedback configuration?

- A) Current-Series Feedback
- B) Voltage-Shunt Feedback
- C) Current-Voltage Feedback**
- D) Current-Shunt Feedback

Answer: (C)

15. On what criteria does the feedback amplifier are classified?

- A) Signal Fed Back To Input
- B) Signal Applied To Input
- C) Signal Fed Back To Output
- D) None of the mentioned**

Answer: (D)

16. Select the specifications that implies the inverting amplifier?

- A) $V_1 = -3V, V_2 = -4V$
- B) $V_1 = -2V, V_2 = 3V$
- C) $V_1 = 5V, V_2 = 15V$
- D) $V_1 = 0v, V_2 = 5v$**

Answer: (D)

17. Given an op-amp whose gain is unknown but the output is saturated, which of the following is not possible?

- A) No Feedback Is Being Applied
- B) Negative Feedback Is Applied While Input Is More Than $-V_{sat}/A_{ol}$**
- C) Positive Feedback Is Applied
- D) Negative feedback is applied while the input is more than V_{sat}/A_{OL}

Answer: (B)

18. The output of a particular Op-amp increases 8V in 12 μ s. The slew rate is

- A) 90 V/ μ s
- B) 0.67 V/ μ s**
- C) 1.5 V/ μ s
- D) None of these

Answer : (B)

19. The tail current of a differential amplifier is

- A) Half of either collector current
- B) Equal to either collector current
- C) Two times either collector current**
- D) Equal to the difference in base currents

Answer : (C)

20. In the expression $v_o = -Av_n$, A is called _____

- A) Closed Loop Gain
- B) Closed Loop Fault
- C) Open Loop Fault
- D) Open loop gain**

Answer: (D)

21. The capacitor doesn't allow sudden changes in _____

- A) Voltage**
- B) Current

- C) Resistance
D) Capacitance

Answer: (A)

22. A voltage across a capacitor of 0.5F is defined by

$$V(t) = [0, t < 0$$

$$2t, 0 < t < 2s$$

$$4e^{-(t-2)}, t > 2s, \text{ Find } i(t).$$

- A) $-2e^{-(T-2)} \text{ A}$
B) $-4e^{-(T-2)} \text{ A}$
C) $-20e^{-(T-2)} \text{ A}$
D) $-12e^{-(T-2)} \text{ A}$

Answer: (A)

23. For an ideal non-inverting operational amplifier having finite gain (A), the ratio of output voltage (v_o) to input voltage (v_i) is (given R_2 is the feedback resistance)

- A) $(1+R_2/R_1)/(1+((1+R_2/R_1)/A))$
B) $(R_2/R_1)/(((1+R_2/R_1)/A))$
C) $(1+R_2/R_1)/(((1+R_2/R_1)/A))$
D) $(R_2/R_1)/(1+((1+R_2/R_1)/A))$

Answer: (A)

24. The gain for an ideal non-inverting operational amplifier is (given R_2 is the feedback resistance)

- A) $R_2/R_1 - 1$
B) R_2/R_1
C) $-R_2/R_1$
D) $R_2/R_1 + 1$

Answer: (D)

25. For designing a non-inverting amplifier with a gain of 2 at the maximum output voltage of 10 V and the current in the voltage divider is to be $10\ \mu\text{A}$ the resistance required are R_1 and R_2 where R_2 is used to provide negative feedback. Then

A) $R_1 = 0.5\ \text{M}\Omega$ AND $R_2 = 0.5\ \text{M}\Omega$

B) $R_1 = 0.5\ \text{k}\Omega$ AND $R_2 = 0.5\ \text{k}\Omega$

C) $R_1 = 5\ \text{M}\Omega$ AND $R_2 = 5\ \text{M}\Omega$

D) $R_1 = 5\ \text{k}\Omega$ and $R_2 = 5\ \text{k}\Omega$

Answer: (A)