



## Department of Electrical and Electronics Engineering

### EE8451-Linear Integrated Circuits & Applications

#### Unit III - MCQ Bank

1. Strain gage is an example of which device?  
A) **Transducer**  
B) Voltage Follower  
C) Integrator  
D) Differentiator  
Answer: (A)
2. In an instrumentation amplifier using transducer bridge, which device measure the change in physical energy  
A) **Resistive Transducer**  
B) Indicating Meter  
C) Capacitive Transducer  
D) Inductor Circuit  
Answer: (A)
3. General purpose op-amps are used in applications as  
A) Instrumentation Amplifier  
B) **Differential Instrumentation Amplifier**  
C) Inverting Instrumentation Amplifier  
D) Non-inverting instrumentation amplifier  
Answer: (B)
4. 4. Consider a thermistor having the following specifications:  $R_F=150k\Omega$  at a reference temperature of  $35^\circ\text{C}$  and temperature coefficient of resistance =  $25^\circ\text{C}$ . Determine the change in resistance at

100°C.

**A) -1.625MΩ**

B) 9.75MΩ

C) 4.78MΩ

D) None of the mentioned

Answer: (A)

5. Express the equation for transducer bridge, if all the resistor values are equal

A)  $v = -(\Delta r \times v_{dc}) / (2 \times r + \Delta r)$

B)  $v = -(\Delta r \times v_{dc}) / 2 \times (r + \Delta r)$

C)  $v = -v_{dc} / [2 \times (2 \times r + \Delta r)]$ .

**D)  $v = -(\Delta R \times V_{dc}) / [2 \times (2 \times R + \Delta R)]$ .**

Answer: (D)

6. Which material is used for photoconductive cells?

A) Germanium

**B) Cadmium Sulphide**

C) Lithium

D) Phosphorous

Answer: (B)

7. How a differential instrumentation amplifier using transducer bridge can be used as a temperature controller?

A) Increase Room Temperature

**B) Replaces Calibrated Meter With Relay**

C) Change The Bridge Resistance

D) Replace Thermistor By Light Intensity Meter

Answer: (B)

8. Which of the following functions does the antilog computation required to perform continuously with log-amps?

- A)  $\ln(X)$   
 B)  $\log(X)$   
 C)  $\sinh(X)$   
**D) All of the mentioned**

Answer: (D)

9. Find the output voltage of the log-amplifier

- A)  $V_o = -(Kt) \times \ln(V_i/V_{ref})$   
**B)  $V_o = -(Kt/Q) \times \ln(V_i/V_{ref})$**   
 C)  $V_o = -(Kt/Q) \times \ln(V_{ref}/V_i)$   
 D)  $V_o = (kT/q) \times \ln(V_i/V_{ref})$


Answer: (B)

10. The input voltage, 6v and reference voltage, 4 v are applied to a log-amp with saturation current and temperature compensation. Find the output voltage of the log-amp?

- A)  $6.314(Kt/Q)V$   
 B)  $0.597(Kt/Q)V$   
**C)  $0.405(Kt/Q)V$**   
 D)  $1.214(kT/q)v$

Answer: (C)

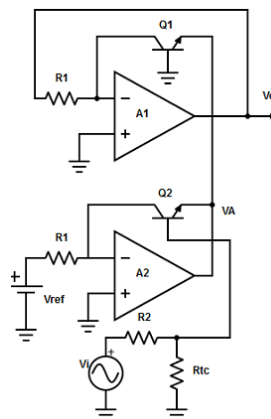11. Determine the output voltage for the given circuit



A)  $V_o = V_{ref}/(10^{-K'v_i})$

B)  $V_o = V_{ref}+(10^{-K'v_i})$

C)  $V_o = V_{ref}\times(10^{-K'v_i})$

D)  $V_o = V_{ref}-(10^{-K'v_i})$

Answer: (C)

12. Determine output voltage of analog multiplier provided with two input signal  $V_x$  and  $V_y$ .

A)  $V_o = (V_x \times V_x) / V_y$

B)  $V_o = (V_x \times V_y / V_{ref}$

C)  $V_o = (V_y \times V_y) / V_x$

D)  $V_o = (V_x \times V_y) / V_{ref}^2$

Answer: (B)

13. An input of  $V\sin\omega t$  is applied to an ideal frequency doubler. Compute its output voltage?

A)  $V_o = [(V_x \times V_y) / V_{ref}^2] \times [1 - \cos 2\omega t / 2]$ .

B)  $V_o = [(V_x^2 \times V_y^2) / V_{ref}] \times [1 - \cos 2\omega t / 2]$ .


C)  $V_o = [(V_x \times V_y)^2 / V_{ref}] \times [1 - \cos 2\omega t / 2]$ .

D)  $V_o = [(V_x \times V_y) / (V_{ref})] \times [1 - \cos 2\omega t / 2]$ .

Answer: (D)

14. Find the output voltage for the squarer circuit given below, choose input frequency as 10kHz and

$V_{ref} = 10v$

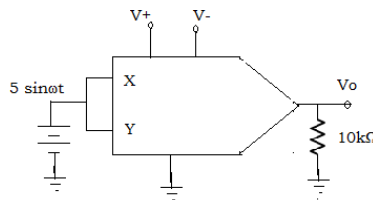

15.

A)  $V_o = 5.0 - (5.0 \times \cos 4\pi \times 10^4 t)$

B)  $V_o = 2.75 - (2.75 \times \cos 4\pi \times 10^4 t)$

C)  $V_o = 1.25 - (1.25 \times \cos 4\pi \times 10^4 t)$

D) None of the mentioned


Answer: (C)

15. Express the output voltage equation of divider circuit

- A)  $V_o = -(V_{ref}/2) \times (V_z/V_x)$
- B)  $V_o = -(2 \times V_{ref}) \times (V_z/V_x)$
- C)  $V_o = -(V_{ref}) \times (V_z/V_x)$**
- D)  $V_o = -V_{ref}^2 \times (V_z/V_x)$

Answer: (C)

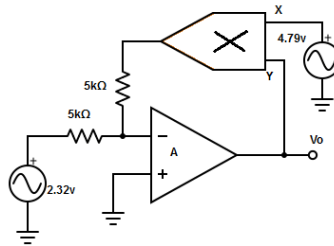16. Find the input current for the circuit given below.



- A)  $I_Z = 0.5372\text{mA}$
- B)  $I_Z = 1.581\text{mA}$**
- C)  $I_Z = 2.436\text{mA}$
- D)  $I_Z = 9.347\text{mA}$

Answer: (B)

17. Which circuit allows to double the frequency?

- A) Frequency doubler**
- B) Square doubler
- C) Double multiplier
- D) All of the mentioned

Answer: (A)

18. Find the voltage range at which the multiplier can be used as a squarer circuit?

- A)  $0 - V_{in}$
- B)  $V_{ref} - V_{in}$**

- C)  $0 - V_{\text{ref}}$   
 D) All of the mentioned

Answer: (C)

19. Which circuit can be used to take square root of a signal?

- A) **Divider circuit**  
 B) Multiplier circuit  
 C) Squarer circuit  
 D) None of the mentioned

Answer: (A)

20. A square root circuit build from multiplier is given an input voltage of 11.5v. Find its corresponding output voltage?

- A) 11v  
 B) 15v  
 C) 13v  
 D) **Cannot be determined**

Answer: (D)

21. In a first order high pass filter, frequencies higher than low cut-off frequencies are called

- A) Stop band frequency  
 B) **Pass band frequency**  
 C) Centre band frequency  
 D) None of the mentioned

Answer: (B)

22. Determine the expression for output voltage of first order high pass filter?

- A)  $V_O = [1 + (R_F / R_1)] \times [(j2\pi fRC) / (1 + j2\pi fRC)] \times V_{in}$   
 B)  $V_O = [-(R_F / R_1)] \times [(j2\pi fRC) / (1 + j2\pi fRC)] \times V_{in}$   
 C)  $V_O = \{ [1 + (R_F / R_1)] \times [1 / (1 + j2\pi fRC)] \} \times V_{in}$   
 D) None of the mentioned

Answer: (A)

23. The internal resistor of the second order high pass filter is equal to  $10\text{k}\Omega$ . Find the value of feedback resistor?

A)  $6.9\text{k}\Omega$

**B)  $5.86\text{k}\Omega$**

C)  $10\text{k}\Omega$

D)  $12.56\text{k}\Omega$

Answer: (B)

24. Determine the expression for time period of a square wave generator

A)  $T = 2RC \ln \left[ \frac{R_1 + R_2}{R_2} \right]$ .

**B)  $T = 2RC \ln \left[ \frac{2R_1 + R_2}{R_2} \right]$ .**

C)  $T = 2RC \ln \left[ \frac{R_1 + 2R_2}{R_2} \right]$ .

D)  $T = 2RC \ln \left[ \frac{R_1 + R_2}{2R_2} \right]$ .

Answer: (B)

25. What will be the frequency of output waveform of a square wave generator if  $R_2 = 1.16 R_1$ ?

A)  $f_o = (1/2RC)$

**B)  $f_o = (\ln/2RC)$**

C)  $f_o = (\ln/2 \times \sqrt{RC})$

D)  $f_o = (\ln/\sqrt{2RC})$

Answer: (B)