



Department of Electrical and Electronics Engineering

EE8601 – SOLID STATE DRIVES

UNIT II

CONVERTER /CHOPPER FED DC MOTOR DRIVE

1. RLE load is a voltage stiff load.

- a) True
- b) False**

Answer: b

2. In Half-wave uncontrolled rectifier calculate the average value of the voltage if the supply is $23\sin(50t)$.

- a) 7.32 V**
- b) 8.32 V
- c) 9.32 V
- d) 7.60 V

Answer: a

3. In Half-wave controlled rectifier calculate the average value of the voltage if the supply is $10\sin(50t)$ and firing angle is 30° .

- a) 2.32 V
- b) 2.97 V**
- c) 4.26 V
- d) 5.64 V

Answer: b

4. Calculate the extinction angle in purely inductive load if the firing angle is $\pi/4$.

- a) 315°**

- b) 145°
- c) 345°
- d) 285°

Answer: a

5. Calculate the conduction angle in purely inductive load if the firing angle is $\pi/2$.

- a) 205°
- b) 175°
- c) **180°**
- d) 195°

Answer: c

6. RLE load is also known as DC motor load.

- a) **True**
- b) False

Answer: a

7. In single phase RLE load, calculate the voltage across the thyristor when current decays to zero using the data: $(V_s)_{r.m.s}=220$ V, $f=40$ Hz, $R=1$ Ω , $E=90$ V, $\beta=230^\circ$.

- a) **-328.33 V**
- b) -325.48 V
- c) -254.85 V
- d) -284.48 V

Answer: a

8. Calculate the displacement factor if the fundamental voltage is $24\sin(140\pi t-240^\circ)$ and fundamental current is $47\sin(140\pi t-120^\circ)$.

- a) **-0.5**
- b) -0.7
- c) 0.9
- d) 0.4

Answer: a

9. Calculate the PIV for the Mid-point configuration of Full-wave rectifier if the peak value of the supply voltage is 311.

- a) **622 V**
- b) 620 V
- c) 624 V
- d) 626 V

Answer: a

10. Calculate the average value of the current through the thyristor in case of 1- Φ Full wave bridge rectifier if the value of the load current is 42 A.

- a) **21 A**
- b) 12 A
- c) 14 A
- d) 16 A

Answer: a

11. Calculate the r.m.s value of the current through the thyristor in case of 1- Φ Full wave bridge rectifier if the value of the load current is 2 A.

- a) **1.414 A**
- b) 1.214 A
- c) 1.347 A
- d) 1.657 A

Answer: a

12. Calculate the value of THD value for 1- Φ Full wave bridge rectifier.

- a) **48.43 %**
- b) 47.25 %
- c) 49.26 %
- d) 50.48 %

Answer: a

13. Calculate the value of the Input power factor for 1- Φ Full wave bridge rectifier if the firing angle value is 45° .

- a) .65
- b) .64
- c) .61
- d) .63**

Answer: d

14. Calculate the value of the fundamental displacement factor for 1- Φ Full wave bridge rectifier if the firing angle value is 60° .

- a) .5**
- b) .4
- c) .2
- d) .8

Answer: a

15. Calculate the value of the fundamental displacement factor for 1- Φ Full wave semi-converter if the firing angle value is 20° .

- a) .82
- b) .98**
- c) .74
- d) .26

16. In Half-wave controlled rectifier calculate the average value of the voltage if the supply is $13\sin(25t)$ and firing angle is 13° .

- a) 4.08 V**
- b) 4.15 V
- c) 3.46 V
- d) 5.48 V

Answer: a

17. Calculate the extinction angle in purely inductive load if the firing angle is 13° .

- a) 328°
- b) 347°**
- c) 349°
- d) 315°

Answer: b

18. Calculate the conduction angle in purely inductive load if the firing angle is 165° .

- a) 78°
- b) 55°
- c) 30°**
- d) 19°

Answer: c

19. R-L-C underdamped loads are generally lagging power factor loads.

- a) True
- b) False**

Answer: b

20. In Half-wave uncontrolled rectifier calculate the average value of the voltage if the supply is $3\sin(5t)$.

- a) .95 V**
- b) .92 V
- c) .93 V
- d) .94 V

Answer: a

21. In Half-wave uncontrolled rectifier calculate the r.m.s value of the voltage if the supply is $89\sin(41t)$.

- a) 91.5 V
- b) 44.5 V**
- c) 25.1 V
- d) 15.1 V

Answer: b

22. In Half-wave uncontrolled rectifier calculate the power dissipation across the $8\ \Omega$ resistor if the supply is $29\sin(22t)$.

- a) 26.2 W**
- b) 24.2 W
- c) 26.1 W
- d) 29.1 W

Answer: a

23. The conduction period of diode in Half-wave uncontrolled rectifier for resistive load is

-
- a) π**
 - b) 2π
 - c) 3π
 - d) 4π

Answer: a

24. In Half-wave uncontrolled rectifier calculate the average value of the current for $3\ \Omega$ resistive load if the supply is $34\sin(11t)$.

- a) 3.6 A**
- b) 2.6 A
- c) 2.5 A
- d) 3.1 A

Answer: a

25. In Half-wave controlled rectifier calculate the average value of the current for 2.5Ω resistive load if the supply is $\sin(5.2t)$ and firing angle is 26° .

- a) 0.8 V
- b) 0.15 V
- c) **0.12 V**
- d) 0.21 V

Answer: c

26. Calculate the circuit turn-off time for Half-wave controlled rectifier for a $\omega=5$ rad/sec for resistive load.

- a) **.62 sec**
- b) .42 sec
- c) .58 sec
- d) .64 sec

Answer: a

27. Calculate the string efficiency if the de-rating factor is .429.

- a) 48.1 %
- b) **57.1 %**
- c) 47.8 %
- d) 46.5 %

Answer: b

28. Calculate the output frequency for the six-pulse converter if the supply frequency is 10 Hz.

- a) 40 Hz
- b) 30 Hz
- c) **60 Hz**
- d) 80 Hz

Answer: c

29. Calculate the pulse number if the supply frequency is 2π and the output frequency is $\pi \div 6$.

- a) 4

- b) **12**
- c) 16
- d) 8

Answer: b

30. Volt-sec balance method is based on the principle of the energy of conservation.

- a) **True**
- b) False

Answer: a

31. Calculate the value of the Input power factor for 1- Φ Full wave bridge rectifier if the firing angle value is 39° .

- a) **.69**
- b) .59
- c) .78
- d) .15

Answer: a

32. Calculate the value of the fundamental displacement factor for 1- Φ Full wave bridge rectifier if the firing angle value is 38° .

- a) .22
- b) **.78**
- c) .33
- d) .44

Answer: b

33. Calculate the value of the fundamental displacement factor for 1- Φ Full wave semi-converter if the firing angle value is 69° .

- a) .48
- b) .24
- c) **.82**

d) .88

Answer: c

34. Calculate the fundamental component of source current in 1- Φ Full wave bridge rectifier for load(Highly inductive) current=3.14 A.

- a) **2.82 A**
- b) 1.45 A
- c) 3.69 A
- d) 4.78 A

Answer: a

35. Calculate the circuit turn-off time for 1- Φ Full wave bridge rectifier for $\alpha=145^\circ$. Assume the value of $\omega=5$ rad/sec.

- a) 84.9 msec
- b) 94.5 msec
- c) 101.2 msec
- d) **87.2 msec**

Answer: d

36. Calculate the fundamental component of source current in 1- Φ Full wave bridge rectifier for the load(Highly inductive) current=78 A.

- a) **78 A**
- b) 45 A
- c) 69 A
- d) 13 A

Answer: a

37. Calculate the r.m.s value of source current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=51.2 A and $\alpha=15^\circ$.

- a) 10.53 A
- b) 14.52 A
- c) 44.92 A

d) **49.02 A**

Answer: d

38. Calculate the r.m.s value of thyristor current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=2.2 A and $\alpha=155^\circ$. (Asymmetrical configuration)

a) .58 A

b) **.57 A**

c) .51 A

d) .52 A

Answer: b

39. Calculate the r.m.s value of diode current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=5.1 A and $\alpha=115^\circ$. (Asymmetrical configuration)

a) 4.21 A

b) **4.61 A**

c) 4.71 A

d) 4.52 A

Answer: b

40. Calculate the average value of thyristor current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=25.65 A and $\alpha=18^\circ$. (Asymmetrical configuration)

a) **11.54 A**

b) 12.15 A

c) 15.48 A

d) 14.52 A

Answer: a

41. Calculate the average value of diode current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=75.2 A and $\alpha=41^\circ$. (Asymmetrical configuration)

a) **46.16 A**

b) 42.15 A

c) 41.78 A

d) 41.18 A

Answer: a

42. Calculate the average value of diode current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=5.2 A and $\alpha=11^\circ$. (F.D configuration)

a) .32 A

b) .31 A

c) .25 A

d) .27 A

Answer: b

43. Calculate the r.m.s value of diode current in 1- Φ Full wave semi-converter for the load (Highly inductive) current=.2 A and $\alpha=74^\circ$. (F.D configuration)

a) .154 A

b) .248 A

c) .128 A

d) .587 A

Answer: c

44. Diodes in 1- Φ Full wave semi-converter protects the thyristor from short-circuiting.

a) True

b) False

Answer: a

45. The problem of short-circuiting in 1- Φ Full wave semi-converter is very common.

a) True

b) False

Answer: a

46. For $\alpha > 90^\circ$, 3- Φ Full wave bridge rectifier acts as a natural commutated inverter.

- a) **True**
- b) False

Answer: a

47. What is the formula for output voltage for 3- Φ Full wave bridge rectifier for R-L load?

- a) $3V_{ml}(\cos(\alpha))\div 2\pi$
- b) **$3V_{ml}(\cos(\alpha))\div \pi$**
- c) $2V_{ml}(\cos(\alpha))\div \pi$
- d) $6V_{ml}(\cos(\alpha))\div \pi$

Answer: b

48. The output voltage of 3- Φ Full wave bridge rectifier is six times of 3- Φ Half-wave rectifier.

- a) True
- b) **False**

Answer: b

49. What is the formula for output voltage for 3- Φ Full wave bridge rectifier for R load for $\alpha < 60^\circ$?

- a) $2V_{ml}(\cos(\alpha))\div \pi$
- b) $3V_{ml}(\cos(\alpha))\div 2\pi$
- c) **$3V_{ml}(\cos(\alpha))\div \pi$**
- d) $6V_{ml}(\cos(\alpha))\div \pi$

Answer: c

50. _____ is the boundary for C.C.M and D.C.M mode in 3- Φ Full wave bridge rectifier for R load.

- a) **60°**
- b) 10°
- c) 80°
- d) 50°

Answer: a

51. What is the formula for output voltage for 3- Φ Full wave bridge rectifier for R load for $\alpha > 60^\circ$?

- a) $2V_{ml}(1+\cos(\alpha+60^\circ))\div\pi$
- b) $3V_{ml}(1+\cos(60^\circ+\alpha))\div2\pi$
- c) **$3V_{ml}(1+\cos(60^\circ+\alpha))\div\pi$**
- d) $6V_{ml}(\cos(\alpha))\div\pi$

Answer: c

52. Calculate the r.m.s value of thyristor current in 3- Φ Full wave converter for the load current=4 A and $\alpha=12^\circ$.

- a) **2.3 A**
- b) 2.5 A
- c) 2.7 A
- d) 2.9 A

Answer: a

53. Calculate the average value of thyristor current in 3- Φ Full wave converter for the load current=9 A and $\alpha=26^\circ$.

- a) 4 A
- b) 5 A
- c) 7 A
- d) **3 A**

Answer: d

54. Calculate the De-rating factor if the string efficiency is 16 %.

- a) **.84**
- b) .44
- c) .5
- d) .6

Answer: a

55. Full form of MOSFET is _____

- a) Metal oxide silicon field effect transistor
- b) Metal oxide semiconductor field effect transistor**
- c) Metal oxide settle field effect transistor
- d) Metal oriented silicon field effect transistor

Answer: b

56. Full form of FET is _____

- a) Field effect transistor**
- b) Field engage transistor
- c) Field effect terminal
- d) Fire engage transistor

Answer: a

57. Calculate the compensator rating required for $\sin(\Phi)=.13$.

- a) 0.45 P.U
- b) 0.12 P.U
- c) 0.13 P.U**
- d) 0.82 P.U

Answer: c

58. Full form of DIAC is _____

- a) Digital Alternating current
- b) Discrete Alternating current
- c) Diode for Alternating current**
- d) Digital Alternating counter

Answer: c

59. Which harmonic is not present in 3- Φ fully controlled rectifier?

- a) **81st harmonic**
- b) 15th harmonic
- c) 17th harmonic
- d) 11th harmonic

Answer: a

60. Fifth lowest order harmonic present in 3- Φ fully controlled rectifier is _____

- a) 15th
- b) **17th**
- c) 13th
- d) 12th

Answer: b.

61. Choppers are used to control the DC voltage level.

- a) **True**
- b) False

Answer: a

62. Which one of the following device is uncontrolled?

- a) SCR
- b) MOSFET
- c) **Diode**
- d) TRIAC